

21/5/22  
21/5/22

**PILLAI COLLEGE OF ENGINEERING, NEW PANVEL**  
(Autonomous) (Accredited 'A+' by NAAC)  
**END SEMESTER EXAMINATION**  
**SECOND HALF 2021**

17-11  
m1

Annex 18

210491

BRANCH: FE (ECS /EXTC )

Subject: Basic Electrical Engineering

Max. Marks: 60

N.B 1. Q.1 is compulsory

2. Attempt any two from the remaining three questions


Time: 02.00 Hours  
Date: 13-04-2022

Q.1.	Attempt all	M	BT	CO
	Calculate the mesh currents in the given circuit.			
a)		5	4	1
	$I_1 = 1.45 A$ $I_2 = 1.873 A$ $I_3 = 10 A$			
b)	Derive average and RMS values of an alternating voltage in terms of maximum value.	5	1	3
c)	A balanced load of phase impedance $100\Omega$ and power factor of 0.5(lag) is connected in delta to a 415V, 3-phase supply. Calculate Phase voltage, Line voltage, Phase current, line current and power consumed. $V_{pb} = \sqrt{3} \times 415V$ $I_{pb} = 1.20$ $I_{pb} = 4.15A$ $I_L = 7.19$	5	4	5
d)	Draw a series R-L-C circuit and derive the equation of Resonant Frequency. $P = 2580.1$	15	1	4
Q.2.	Attempt all			
	Using Thevenin's Theorem, compute the current through 1 ohm resistor.			
a)		4	3	2
	$I_2 = 2.778 A$ $V_{TH} = 3.85V$ $R_{TH} = 3.61$ $I_L = 0.835 A$			
b)	For a three phase star connection prove that line voltage is $\sqrt{3}$ times phase voltage.	4	1	5
c)	Two impedances A and B are connected in series to an alternating voltage, $V=230\angle 0^\circ$ Volts. The impedance of A is $25+j10$ and B is $35-j10$ . Calculate the power factor and total power dissipated in the circuit. $PF = 1$ $P = 881.667 W$ $Z = 60\Omega$	6	4	4
	$T = 3.833$ ; $P = 881.66$			
		P.	T.	O.

Handwritten scribbles at the top left.

5 129 221.801  
5 153 245.95

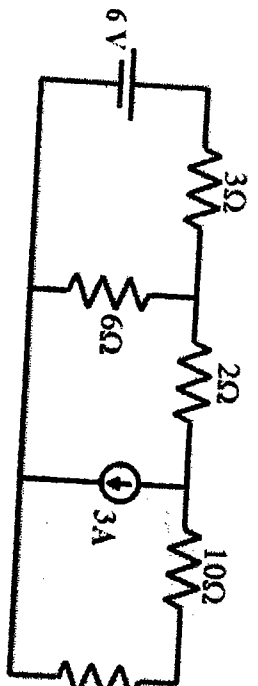
d) Calculate the current flowing through 15Ω resistor using Norton's theorem



$I_1 = 2.285$   
 $I_2 = 2.428$   
 $I_N = I_3 = -0.571$   
 $R_N = 14$   
 $I_{15} = 0.2758$

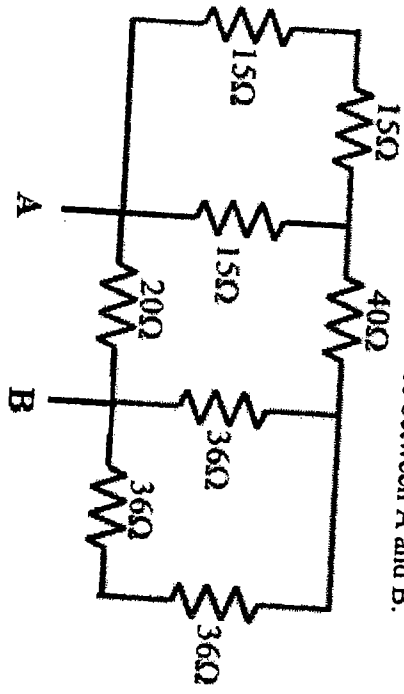Q.3. Attempt all


Compute the equivalent resistance between A and B.



$R_{AB} = 157.4 \Omega$

b) Find the value of current flowing through a 21mH inductor when connected to 230V, 50 Hz, 1-ϕ AC Supply.  $X_L = 6.59$   $I = 35.84 A$

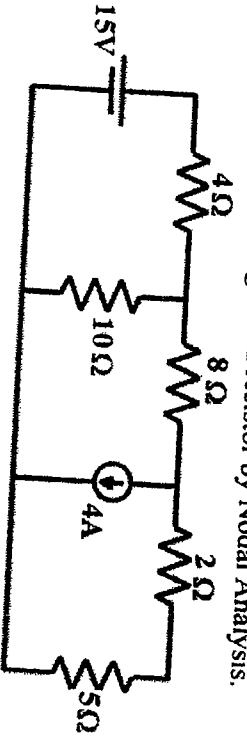c) Find current flowing through 10Ω resistor by Nodal Analysis.




$V_A = 4.52 V$   
 $V_B = -12.82 V$   
 $I_{10} = 0.452 A$

d) Three identical coils having reactance of 15Ω and resistance of 10Ω are connected in star across a 400V three phase line. Calculate:  
 (i) Line current and phase current.  $I_{ph} = 18.05 \angle 56.3$   $V_L = 400$ ;  $V_{ph} = 230.9$   
 (ii) Reading of each Wattmeter connected to measure power.  $W_1 = 4.513 kW$   $W_2 = 329.86$

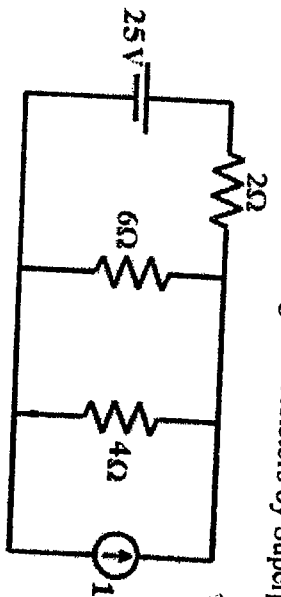Q.4. Attempt all

Find the current flowing through 4Ω resistors by Superposition theorem.




$25V \rightarrow I_{4\Omega} = 3.4 A$   
 $10A \rightarrow I_{4\Omega} = 2.73$   
 $I_4 = 6.15$

b) An alternating voltage is represented by  $v = 141.4 \sin(377t + 0)$  Volts. Find (i) Max Voltage (ii) RMS value (iii) frequency and (iv) Time period.

$V_m = 141.4$   
 $f = 60 Hz$

$T = 0.016$

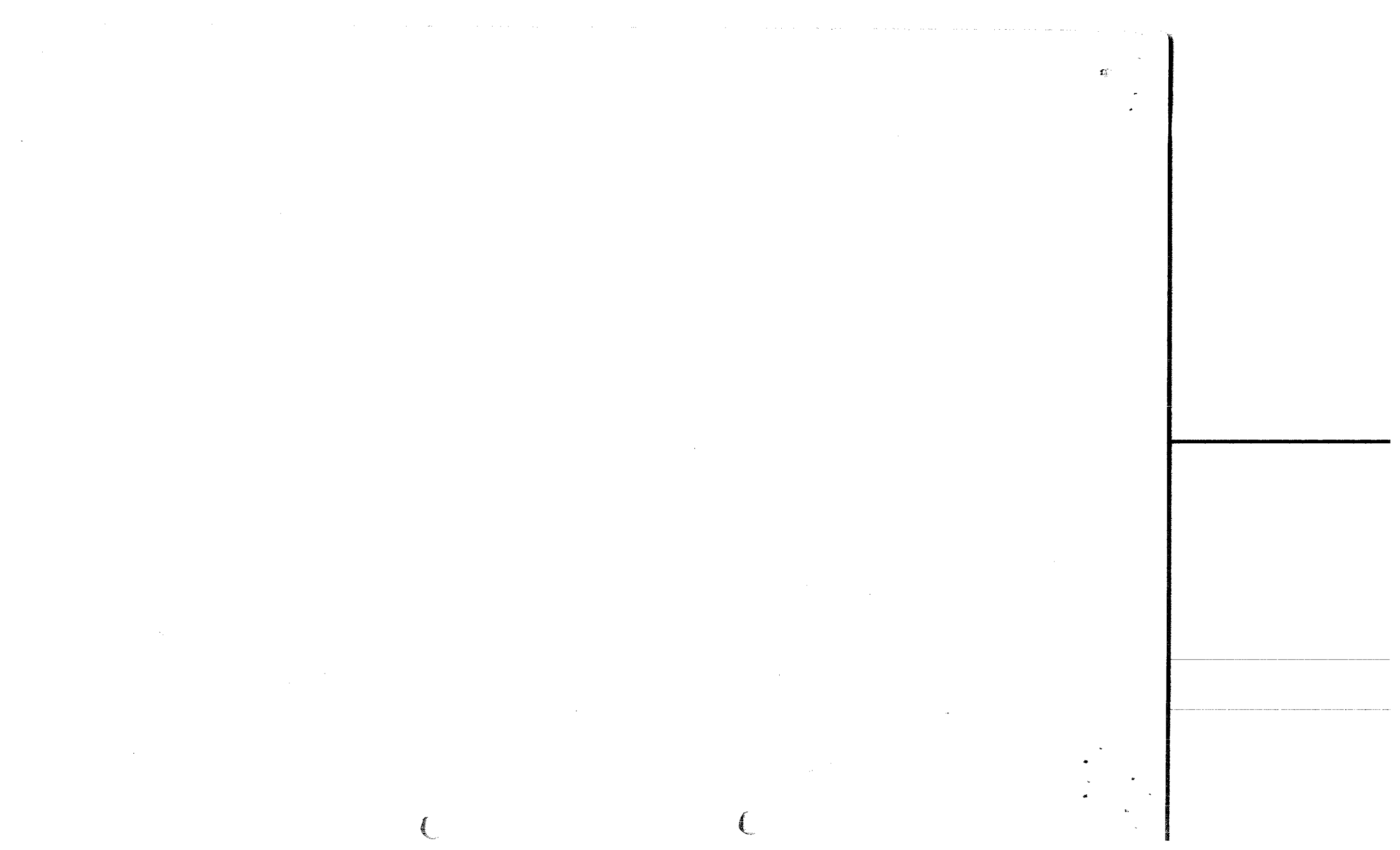


$f_0 = 21.17 \text{ Hz}$

$Z_D = 53.33 \Omega$

$I = 4.3125 \text{ A}$

c)	<p>A circuit has <math>L=0.2\text{H}</math> and inductive resistance <math>25\Omega</math> is connected in parallel with <math>150\mu\text{F}</math> capacitor with variable frequency, <math>230\text{V}</math> supply. Find the resonant frequency and impedance at which the total current taken from the supply is in phase with supply voltage. Also find the value of the supply current and impedance at resonance.</p>	6	3	4
d)	<p>Evaluate the value of R for maximum power transfer and also calculate the maximum power in the load resistor.</p>			

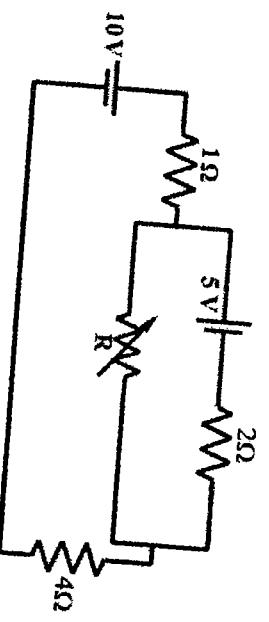

$I = 0.71$   
 $V_{TH} = 6.428$   
 $R_{TH} = 1.428$   
 $P_{max} = 7.233 \text{ W}$

- CO1-Apply basic concepts to analyse D.C circuits.
  - CO2-Apply various D.C network theorems to determine the circuit response/ behaviour.
  - CO3-Apply basic concepts to analyse A.C waveforms.
  - CO4-Evaluate and analyse single phase A.C circuits.
  - CO5-Evaluate and analyse three phase A.C circuits.
  - CO6-Understand the constructional features and operation of electrical machines.
- BT Levels: - 1 Remembering, 2 Understanding, 3 Applying, 4 Analyzing, 5 Evaluating, 6 Creating.
- M-Marks, BT- Bloom's Taxonomy, CO-Course Outcomes.


$\frac{54}{L2}$

*R*

13/04/22

Q1

Q

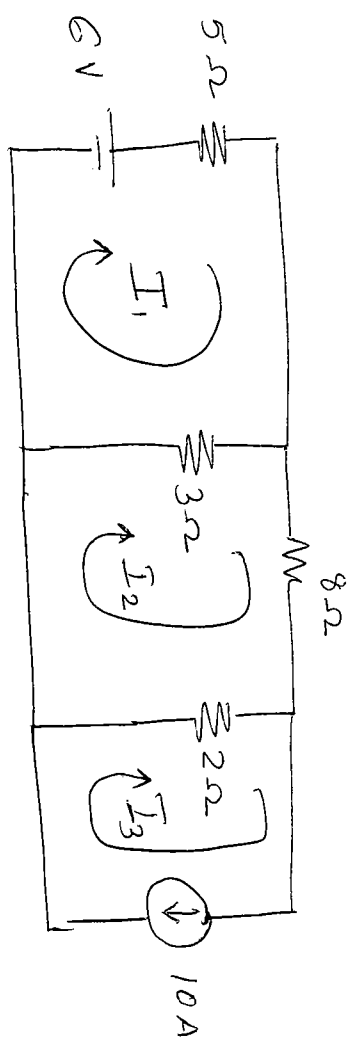

$$6 - 5I_1 - 3C(I_1 - I_2) = 0$$

$$-8I_1 + 3I_2 = -6 \quad \text{--- (1)}$$


$$-3C(I_2 - I_1) - 8I_2 - 2C(I_2 - 10) = 0$$

$$3I_1 - 13I_2 = -20 \quad \text{--- (2)}$$

$$I_1 = 1.45A, \quad I_2 = 1.873A, \quad I_3 = 10A$$

Q1 b

$x = V_m \sin \omega t$

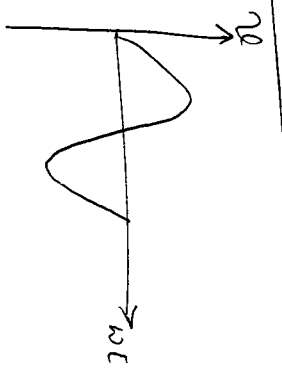

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2(\omega t) d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \left[ \frac{1 - \cos 2\omega t}{2} \right] d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2} \int_0^{2\pi} \frac{1 - \cos 2\omega t}{2} d\omega t} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Q1

c)

$$R = 100 \Omega$$

$$\cos \phi = 0.5$$



$$\phi = 60$$

$$Z_{pb} = 100 \angle 60$$

$$\tan 60 = \frac{X_L}{R}$$

$$= 50 + 86.6j$$

$$X_L = 100 \times \tan 60$$

$$= 173.20 \Omega$$

$$Z = 100 + 173.20j$$

$$Z_{pb} = 200 \angle 60 \Omega$$

$$V_L = V_{pb} = 415 V$$

$$I_{pb} = \frac{415}{200} = 2.075$$

$$I_{pb} = 4.15 A$$

$$I_L = \sqrt{3} I_{pb}$$

$$I_L = 7.18 A$$

$$I_L = 3.594 A$$

$$P = \sqrt{3} V_L I_L \cos \phi$$


$$= \sqrt{3} \times 415 \times 3.594 \times \cos 60$$

$$= 1291.6 W$$

$$P = 1292 W$$

$$\underline{\underline{2580.5 W}}$$

Q2  
A.

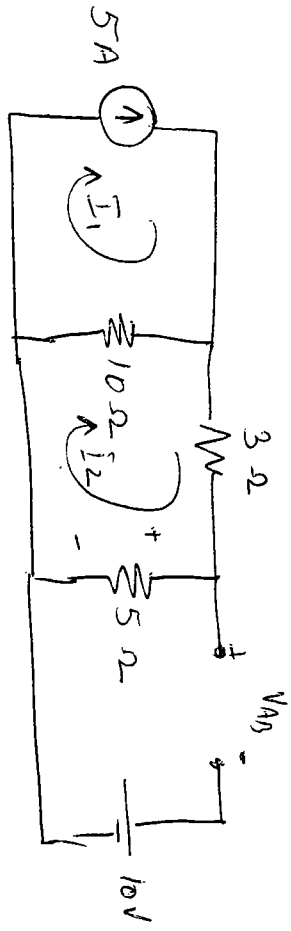

$$-3 I_2 - 5 I_2 - 10 (I_2 - 5) = 0$$

$$-18 I_2 = -50$$

$$I_2 = 2.778 \text{ A}$$

$$V_{AB} = 5 \times 2.778 + 10 = 0$$

$$V_{AB} = 13.85 - 10$$





$$= 3.85 \text{ V}$$

$$V_{TH} = 3.85 \text{ V}$$


$$R_{TH} = 3.61 \Omega$$



$$I_{1\Omega} = 0.8351 \text{ A}$$

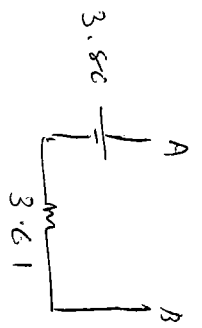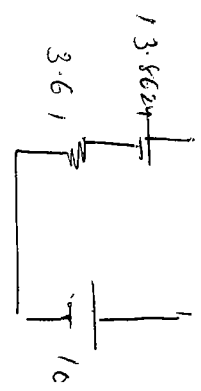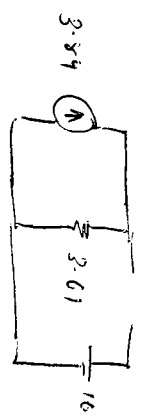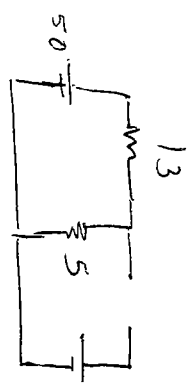

C.

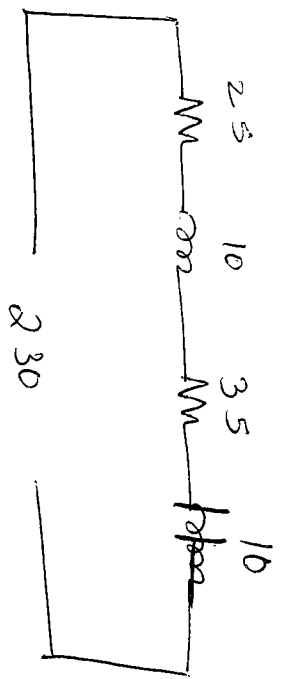

$$Z = 2.5 + j10 + 3.5 - j10$$

$$= 60 \Omega$$


$$pf = \cos \phi$$

$$= 1$$

$$P = 230 \times 3.833 \times \cos 0$$

$$P = \underline{\underline{881.667 \text{ W}}}$$

Q2 d

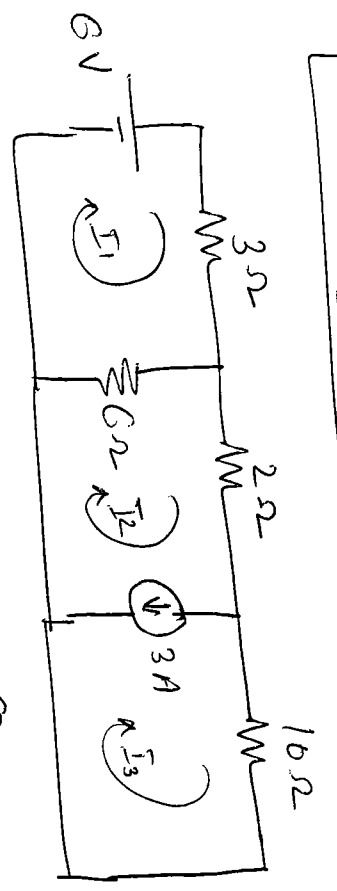

$$I_2 - I_3 = 3 \quad \text{--- (1)}$$

$$6 - 3I_1 - 6(I_1 - I_2) = 0 \quad \text{--- (2)}$$

$$-9I_1 + 6I_2 = -6$$

$$-2I_2 - 10I_3 - 6(I_2 - I_1) = 0 \quad \text{--- (3)}$$


$$6I_1 - 8I_2 - 10I_3 = 0$$

$$I_1 = 2.285 \quad I_2 = 2.428 \quad I_3 = -0.571$$




$$I_N = -0.571 \text{ A}$$

$R_N =$






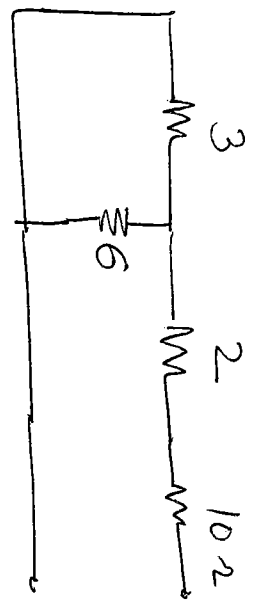


$$R_N = 14 \Omega$$


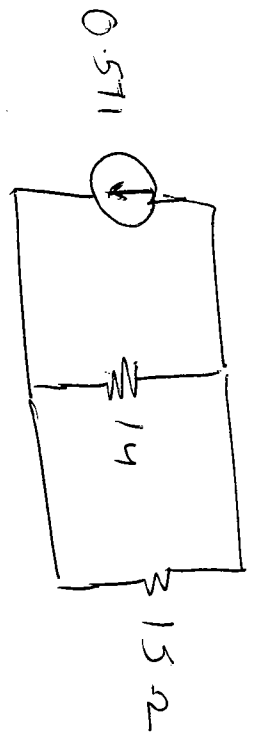


$$I_{15\Omega} = \frac{0.571 \times 14}{14 + 15}$$
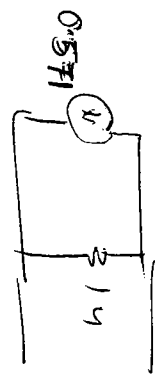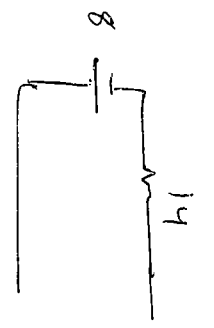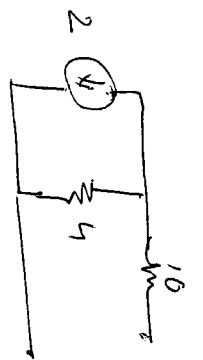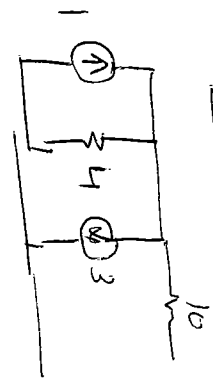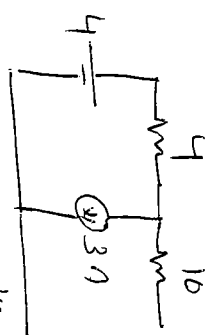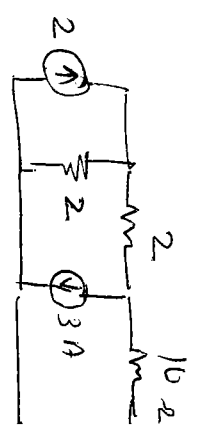
$$I_{15\Omega} = \underline{\underline{0.2756 \text{ A}}}$$



Q2

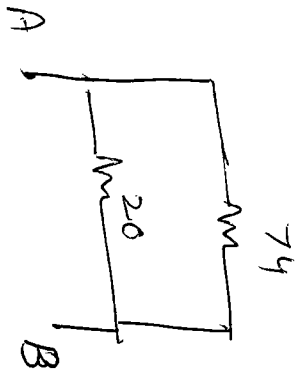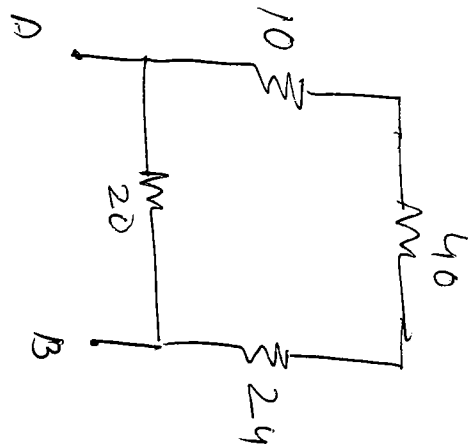

$$R_{AB} = \underline{\underline{15.7446 \Omega}}$$



Q3  
b)

$$X_L = 2\pi \times 50 \times 21 \text{ m}$$

$$\approx 6.597 \Omega$$

$$I = \frac{230}{6.597} = \underline{\underline{34.84 \text{ A}}}$$

Q3C

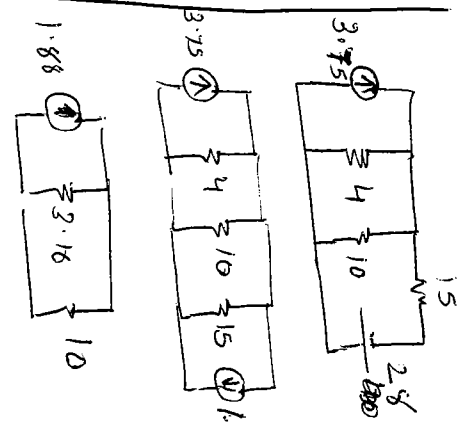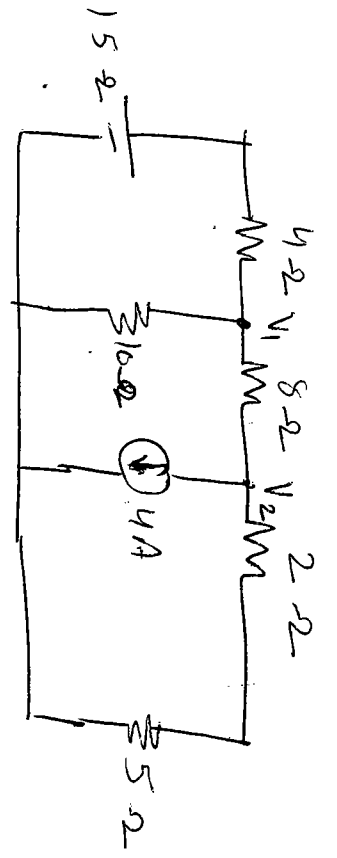

(4)

$$V_1 - 15 + \frac{V_1}{10} + \frac{V_1 - V_2}{8} = 0$$

$$V_1 \left[ \frac{1}{4} + \frac{1}{10} + \frac{1}{8} \right] + V_2 \left[ \frac{-1}{8} \right] = -\frac{15}{4} \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{8} + 4 + \frac{V_2 - 0}{7} = 0$$

$$V_1 \left[ -\frac{1}{8} \right] + V_2 \left[ \frac{1}{8} + \frac{1}{7} \right] = -4 \quad \text{--- (2)}$$

$$V_1 = \underline{\underline{5.576 \text{ V}}} \quad V_2 = \underline{\underline{-8.8076 \text{ V}}}$$

$$I_{10\Omega} = \frac{4.52}{5.576} = \underline{\underline{0.8092 \text{ A}}}$$

Q3 d

$$Z_{ph} = 10 + j15$$


$$= 18.02 \angle ~~33.69~~ 56.30$$

$V_L = 400 \text{ V}$
$V_{ph} = \underline{\underline{230.9 \text{ V}}}$
$I_{ph} = 12.815 \text{ A}$
$I_L = 12.815$

$$\begin{aligned} W_1 &= V_L I_L \cos(30 - \phi) \\ &= 400 \times 12.815 \cdot \cos 3.69 \\ &= 5115.37 \text{ W} \end{aligned}$$

$$\begin{aligned} W_2 &= V_L I_L \cos(90 + \phi) \\ &= 400 \times 12.815 \times \cos 63.69 \\ &= \underline{\underline{2271.98 \text{ W}}} \end{aligned}$$

Q4  
a)

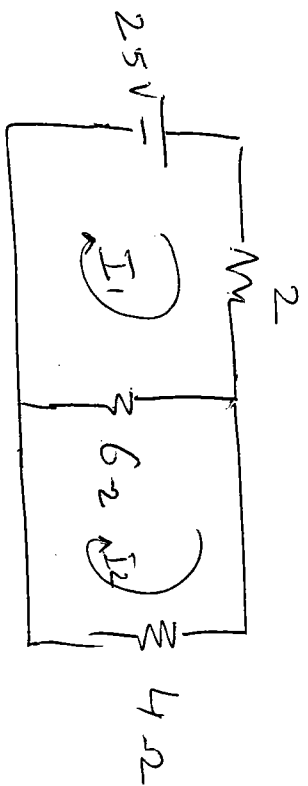

$$25 - 2I_1 - 6(I_1 - I_2) = 0$$


$$-8I_1 + 6I_2 = -25 \quad \text{--- (1)}$$

$$-4I_2 - 6(I_2 - I_1) = 0$$

$$6I_1 - 10I_2 = 0 \quad \text{--- (2)}$$

$$I_1 = 5.68 \quad I_2 = 3.4$$
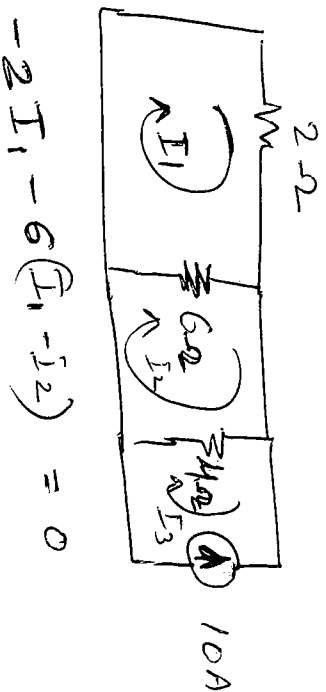
$$I_{4\Omega} = \underline{\underline{3.4 A}}$$



$$-2I_1 - 6(I_1 - I_2) = 0$$

$$-8I_1 + 6I_2 = 0 \quad \text{--- (1)}$$

$$-6(I_2 - I_1) - 4(I_2 + 10) = 0$$


$$6I_1 - 10I_2 = 40 \quad \text{--- (2)}$$

$$I_1 = -5.45 \quad I_2 = -7.27$$

$$I_{4\Omega}'' = I_3 - I_2 \quad (\uparrow)$$

$$= -10 + 7.27$$
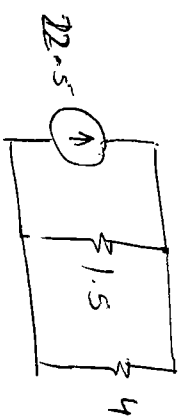
$$I_{4\Omega}'' = 2.73 \quad \downarrow$$



$$I_{4\Omega} = 6.15 A$$

Q4

b

$$V_m = 141.4 \text{ V}$$

$$V_{R_{ms}} = 99.98 \text{ V}$$

$$W = 377$$

$$f = \frac{377}{2\pi} = 60 \text{ Hz}$$

$$\tau = \underline{\underline{0.016 \text{ Sec}}}$$

$$f_a = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Q9c


$$= \frac{1}{2\pi} \sqrt{33333.33 - 15625}$$
$$= \underline{\underline{21.179 \text{ Hz}}}$$

$$Z_D = \frac{L}{RC} = \underline{\underline{53.33 \Omega}}$$

$$I = \frac{230}{Z_D} = \underline{\underline{4.3125 \text{ A}}}$$



Q11

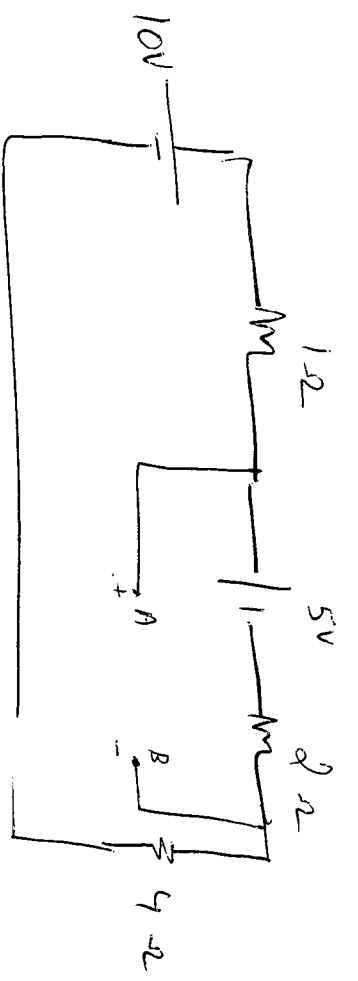

(6)

$$10 - 1I - 5 - 2I - 4I = 0$$

$$5 = 7I$$

$$I = \frac{5}{7}$$

$$V_{AB} = 5 - 2 \times \frac{5}{7} = 0$$

$$V_{AB} = 5 + \frac{10}{7}$$

$$V_{TH} = \underline{\underline{6.428 \text{ V}}}$$

$$R_{TH} = 1.428 \Omega$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \underline{\underline{7.233 \text{ W}}}$$