



PILLAI COLLEGE OF ENGINEERING, NEW PANVEL
(Autonomous) (Accredited 'A+' by NAAC)
END SEMESTER EXAMINATION
SECOND HALF 2021

BRANCH: FE (Mech /Auto)

Subject: Basic Electrical and Electronics Engineering **Time: 02.00 Hours**
Max. Marks: 60 **Date: 13-04-2022**

N.B 1. Q.1 is compulsory

2. Attempt any two from the remaining three questions


Q.I.	Attempt all	M	BT	CO
	Calculate the current flowing through 5Ω resistance using Nodal Analysis.			
a)	$I_{5\Omega} = 2.16 \text{ A} (\downarrow)$	5	4	1
b)	An impedance with two elements in a series connection has the following applied voltage and current: $v(t) = 200 \sin(350t+60^\circ) \text{ V}$, $i(t) = 11.12 \sin(350t+30^\circ) \text{ A}$.	5	4	2
c)	Calculate the supply frequency (in Hz) and the value of circuit elements. $f = 55.4 \text{ Hz}$ $\rho = 15, 58 \Omega$ $L = 0.0256 \text{ H}$			
d)	Three identical coils each $[2.2+j3.6]\Omega$ are connected in star across $430\text{V}, 50\text{Hz } 3\phi$ supply. Calculate i) V_{ph} ii) I_{ph} iii) V_i . iv) I_L v) Power and vi) Power factor. 248.28 58.96 38.96 $2.2 \cdot 89 \mu\text{W}$ 0.521 lag	5	4	3
Q.2.	With a neat diagram, explain the working of a full wave bridge rectifier.	5	5	5
	Attempt all			
	Using source transformation, calculate current through a 3Ω resistor.	4	4	1
a)	$I_{3\Omega} = 3.48 \text{ A} (\downarrow)$	P.	T.	O.

An alternating voltage is represented by $v(t) = 341.22 \sin(260t)$ V. Calculate:

- b)
 (i) Maximum value of the voltage. 341.22 ✓
 (ii) RMS value of this voltage. 241.27 ✓
 (iii) instantaneous value at $t = 3\text{ms}$ 239.97 ✓

- c) With the help of a neat circuit diagram and phasor diagram explain the 2-wattmeter method to measure power in a 3φ balanced delta connected load.

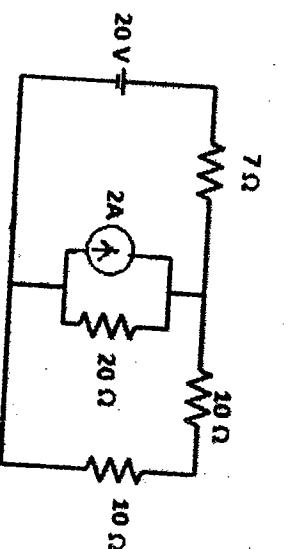- d) Calculate the value of current flowing through the 7Ω resistance using superposition theorem.



$$20V \text{ active } I_{7\Omega} = 1.136A (\rightarrow)$$

$$2A \text{ active } I_{7\Omega} = 6.136A (\leftarrow)$$

$$6$$

$$4$$


$$1$$

Q.3. Attempt all

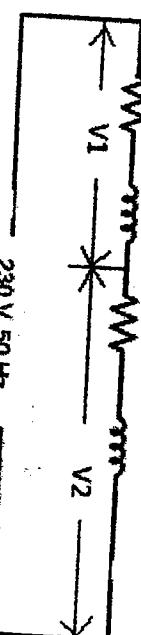- a) State and explain Thevenin's Theorem.


In the circuit shown calculate i) current ii) V_1 and V_2 and iii) Power factor.

$$1.393A \quad 243.23V \quad 42.01V \quad 0.2424 \text{ lag}$$



$$4 \quad 5 \quad 1$$

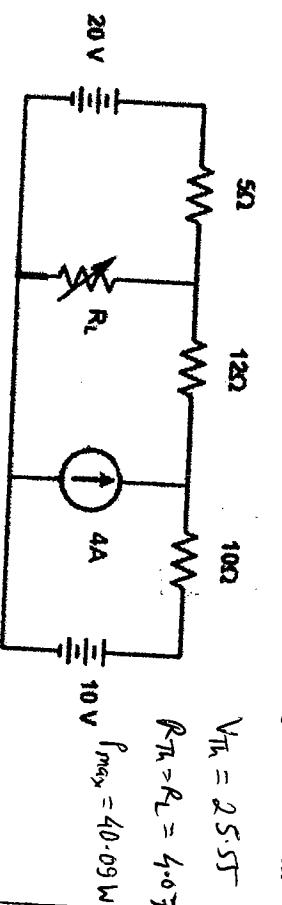- c) Calculate the maximum power transferred to the load resistor for the given circuit.



$$V_{Th} = 25.55$$

$$R_{Th} > R_L = 4.07$$

$$6$$

$$4$$


$$1$$

d) A coil having a resistance of 20Ω and an inductance of $0.02H$ is connected in series with a $60\mu F$ capacitor. An alternating voltage of $230V$ is applied to the circuit. At what value of frequency will the circuit current and supply voltage be in phase? Calculate the value of this current? Also draw the phasor diagram of current and voltage at this frequency.

$$f_r = 145.28 \text{ Hz} \quad I_r = 11.5 \text{ A}$$

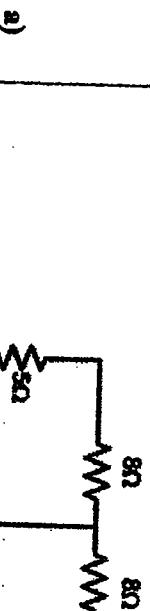Q.4. Attempt all

Calculate the current through 4Ω resistance using Mesh Analysis.




4 4 1

$$I_{4\Omega} = 0.313 \text{ A} (\downarrow)$$

b) Formulate the equation for resonant frequency in a parallel resonance circuit.

4 2

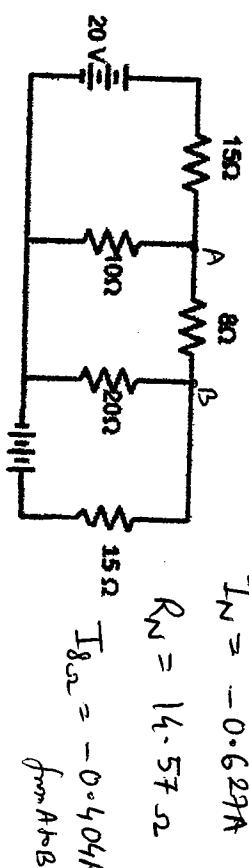c) Using Norton's Theorem, calculate the current in 8Ω resistor.



$$I_N = -0.627 \text{ A}$$

$$R_N = 14.57 \Omega$$

$$I_{8\Omega} = -0.404 \text{ A}$$

from A to B

d) Two impedances $42 + j32$ and $19 - j10$ are connected in parallel across

$200V, 50 \text{ Hz}$, single phase supply. Compute:

- (i) Total impedance of the circuit (ii) Current in each branch in polar form; (iii) power factor of the circuit (iv) Total power consumed by the circuit.

$$0.9839 \angle 26.1^\circ$$

6 3 2

CO1- To evaluate D.C. circuits using network theorems.


CO2- Apply the concept of ac circuit and its resonance phenomena for a given RL, RC and RLC circuit.

CO3- To evaluate 3-Φ AC circuits

CO5- To illustrate the working principle of DC Machine


BT Levels: - 1 Remembering, 2 Understanding, 3 Applying, 4 Analyzing, 5 Evaluating, 6 Creating.

 M-Marks, BT- Bloom's Taxonomy, CO-Course Outcomes.



①

Q.1 a)

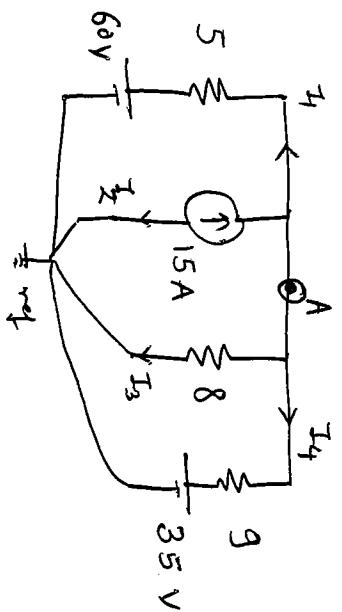

KCL @ node A

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\left[\frac{V_A - 60}{5} \right] + \left[-15 \right] + \left[\frac{V_A - 0}{8} \right] + \left[\frac{V_A - 35}{9} \right] = 0$$

$$V_A \left[5^{-1} + 8^{-1} + 9^{-1} \right] = \frac{60}{5} + 15 + \frac{35}{9}$$

$$V_A \left[5^{-1} + 8^{-1} + 9^{-1} \right] = 30.88$$

$$V_A = 70.82 \text{ V}$$

$$\therefore I_{5\omega} = \left[\frac{V_A - 60}{5} \right] = \left[\frac{70.82 - 60}{5} \right] = 2.16 \text{ A} (\downarrow)$$

Q.1 b)

$$v(t) = 200 \sin(350t + 60^\circ) \quad i(t) = 11.12 \sin(350t + 30^\circ)$$

$$\bar{V} = 141.42 \angle 60^\circ$$

$$\omega = 350 \quad \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{141.42 \angle 60^\circ}{7.86 \angle 30^\circ} = 15.58 + 8.99j$$

$$2\pi f = 350$$

$$f = 55.7 \text{ Hz}$$

Circuit element

$$R = 15.58 \Omega$$

$$X_L = 8.99 \Omega$$

$$\omega L = 8.99$$

$$L = \frac{8.99}{\omega} = \frac{8.99}{350}$$

$$L = 0.0256 \text{ H}$$

Node

Q. 1 C]

Star connection $V_L = \sqrt{3} V_{ph}$, $I_L = I_{ph}$

$$V_L = 430$$

$$f = 50 \text{ Hz}$$

$$Z_{ph} = 2.2 + j 3.6$$

$$Z_{ph} = 4.21 \angle 58.57^\circ$$

$$(i) V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{430}{\sqrt{3}} = [248.26 \text{ V}]$$

$$(ii) I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{248.26}{4.21} = [58.96 \text{ A}]$$

$$(iii) V_L = 430 \text{ V}$$

$$(iv) I_L = I_{ph} = 58.96 \text{ A}$$

$$(v) P = \sqrt{3} V_L I_L \cos \phi \\ = \sqrt{3} \times 430 \times 58.96 \times \cos (58.57^\circ)$$



$$= 22898.37 \text{ W}$$

$$(vi) P_f = 22.89 \text{ kW}$$

$$(vii) P_f = \cos \phi \\ = \cos (58.57^\circ)$$

$$P_f = 0.521 \text{ lag}$$

(2)

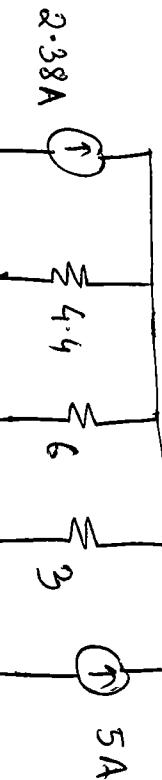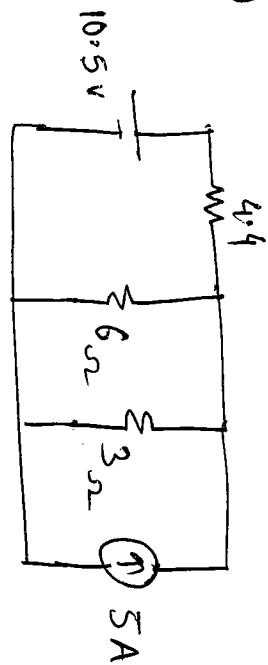Q.2
Q.2(a)

$$I_{3n} = \frac{2.53}{2.53 + 3} \times 7.38$$

$$I_{3n} = 3.48A (\downarrow)$$

Q.2 b) $v(t) = 341.22 \sin(260t)$


(i) $V_m = 341.22 \text{ V}$

(ii) $V_m = \frac{V_m}{\sqrt{2}} = 241.27 \text{ V}$

(iii) $v = 3.41 \cdot 341.22 \times \sin(260 \times 3 \times 10^{-3})$

$$v = 239.97 \text{ V}$$

Q.2 d) ① When 20V is active

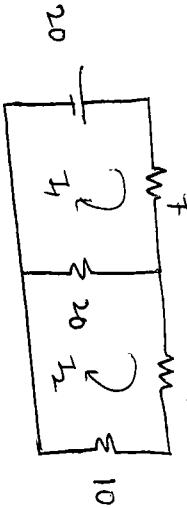

② When 2A is active



calculator
in Rad
Mode

when both
source active

$$I_{7n} = 0$$

$$\begin{aligned} -2I_1 + 20I_2 &= -20 \rightarrow ① \\ 20I_1 - 40I_2 &= 0 \rightarrow ② \end{aligned}$$

$$I_1 = 1.176 \text{ A}$$


$$I_2 = 0.588 \text{ A}$$

$$I_{7n} = 1.176 \text{ A} (\rightarrow)$$

$$I_{7n} = 1.176 \text{ A} (\leftarrow)$$

$$\begin{aligned} I_{7n} &= \frac{V_1}{I} = 1.176 \text{ A} \\ I_{7n} &= 1.176 \text{ A} \end{aligned}$$
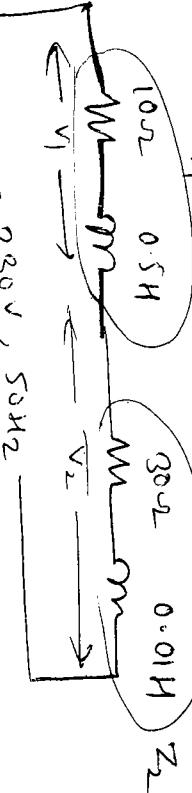
$$Q.3) [b] \quad \begin{array}{c} \text{Z}_1 = 10 + j157.07 \\ \text{Z}_1 = 157.38 L^{86.35^\circ} \end{array}$$




$$\begin{aligned} X_{L_1} &= 2\pi f L = 2\pi \times 50 \times 0.5 \\ &= 157.07 \Omega \\ X_{L_2} &= 2\pi f L = 2\pi \times 50 \times 0.01 \\ &= 3.14 \Omega \end{aligned}$$

$$\begin{aligned} \text{Z}_1 &= 30 + j3.14 \\ \text{Z}_2 &= 30.16 L^{5.97^\circ} \end{aligned}$$

$$\begin{aligned} \text{Z}_T &= \bar{\text{Z}}_1 + \bar{\text{Z}}_2 \\ &= 40.01 + 160.19 j^\circ \\ &= 165.11 L^{75.97^\circ} \end{aligned}$$
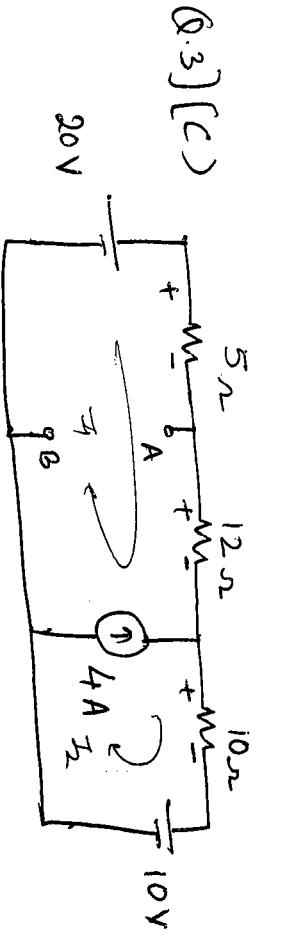
$$\begin{aligned} \text{V}_1 &= \text{I} \text{Z}_1 = 1.393 \times 157.38 \\ &= 219.23 \text{ V} \quad \text{I} = \frac{\text{V}}{\text{Z}_T} = \frac{230}{165.11} = 1.393 \text{ A} \\ \text{P.f} &= \cos \phi = \cos(75.97^\circ) \\ &= 0.2424 \text{ lag.} \end{aligned}$$



$$\text{I}_2 - \text{I}_1 = 4$$

$$-\text{I}_1 + \text{I}_2 = 4 \rightarrow \textcircled{1}$$

$$\begin{aligned} -5\text{I}_1 - 12\text{I}_2 - 10 + 20 &= 0 \\ -17\text{I}_1 - 10\text{I}_2 &= -10 \rightarrow \textcircled{2} \end{aligned}$$

$$R_{AB} = R_{Th} = R_L = 4.07 \Omega$$



$$\begin{aligned} \text{I}_1 &= -1.11 \text{ A} \\ \text{I}_2 &= 2.88 \text{ A} \end{aligned}$$

$$\text{V}_{AB} = 20 - 5(-1.11) = 25.55 \text{ V}$$

$$\boxed{\text{V}_{Th} = \text{V}_{AB} = 25.55 \text{ V}}$$


$$\begin{aligned} P_{max} &= \frac{\text{V}_{Th}^2}{4R_{Th}} \\ &= \frac{(25.55)^2}{4 \times 4.07} \\ &= 40.09 \text{ W} \end{aligned}$$

(Q.3 d)

$$R = 20\Omega$$

$$L = 0.02H$$

$$C = 60\mu F$$

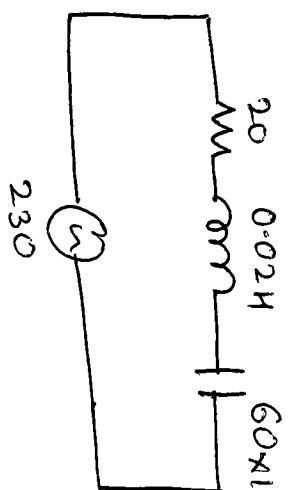


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{0.02 \times 60 \times 10^{-6}}}$$

$$f_r = 145.28 \text{ Hz}$$

$$\rightarrow V \quad \phi = 0^\circ$$

Q.4 a]

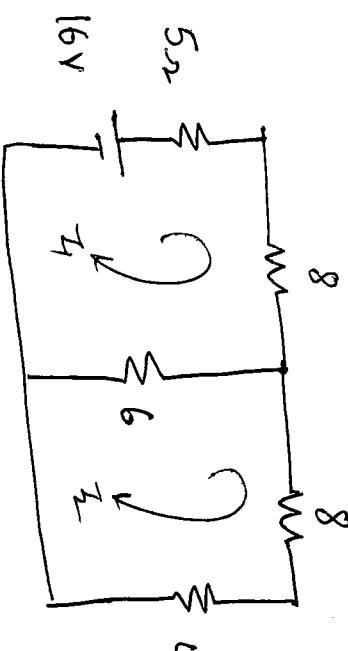


$$-19I_1 + 6I_2 = -16 \rightarrow ①$$

$$6I_1 - 18I_2 = 0 \rightarrow ②$$

$$I_1 = 0.9411 \text{ A}$$

$$I_2 = 0.313 \text{ A}$$
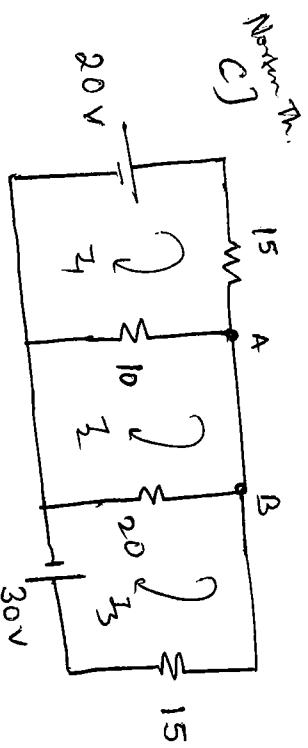
$$I_{45} = 0.313 \text{ A} (\downarrow)$$





$$-25I_1 + 10I_2 = -20 \rightarrow ①$$

$$10I_1 - 30I_2 + 20I_3 = 0 \rightarrow ②$$

$$20I_2 - 35I_3 = 30 \rightarrow ③$$

$$I_N = -0.627 \text{ A} (\rightarrow)$$

$$R_N = 14.531$$

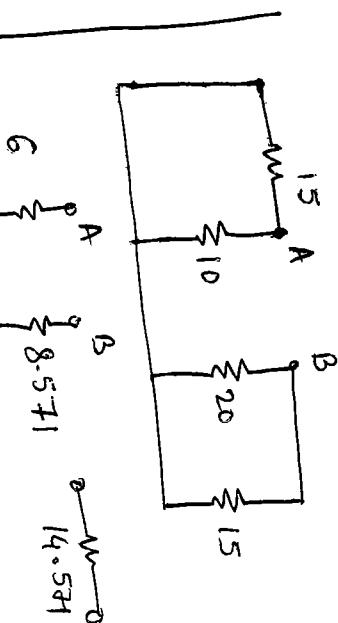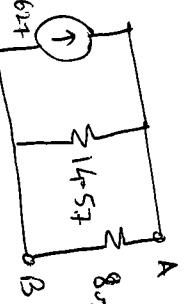

$$I_1 = 0.549 \text{ A}$$

$$I_2 = -0.627 \text{ A}$$


$$I_3 = -1.215 \text{ A}$$

$$I_{85} = \frac{14.57}{14.57 + 8} \times (-0.627)$$

$$I_{85} = -0.404 \text{ A} \text{ from A to B}$$

(3)

Q. 4] (d)

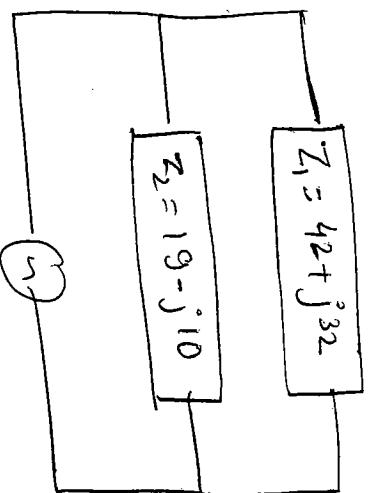

$$\begin{aligned}Z_1 &= 42 + j32 \\Z_2 &= 52.80 \angle 37.30 \\Z_2 &= 19 - j10 \\Z_2 &= 21.47 \angle -27.75\end{aligned}$$

$200 \sqrt{1} \text{ at } 50 \text{ Hz}$

$$\begin{aligned}Z_T &= \frac{Z_1 Z_2}{Z_1 + Z_2} = \\&= \frac{200}{52.80} = 3.78 \text{ A} \\&= 17.20 - j3.12 \\&= 17.48 \angle -10.28 \\I_1 &= \frac{V}{Z_1} = \frac{200}{52.80} = 3.78 \text{ A} \\I_2 &= \frac{V}{Z_2} = \frac{200}{19.47} = 9.31 \text{ A} \\I &= \frac{V}{Z_T} = \frac{200}{21.47} = 9.31 \angle 27.75\end{aligned}$$

$$\begin{aligned}\rho_f &= \cos \phi = \cos(10.28) \\&\geq 0.9839 \text{ (read)} \\&= 2251.27 \text{ W} \\&= 2.0251 \text{ kW}\end{aligned}$$

$$P = V I \cos \phi = 200 \times 11.44 \times \cos(10.28)$$

$$I = \frac{V}{Z_T} = \frac{200}{21.47} = 9.31 \text{ A}$$